



Experiment NO.4 Divider Rules

Aim of experiment

To verify the voltage divider rule (VDR) and the current divider rule (CDR).

Apparatus

1. DC circuit training system.
2. Set of wires.
3. DC Power supply
4. Digital A.V.O. meter.

Theory

Voltage Divider Rule

The Voltage Divider Rule (VDR) states that the voltage across an element or across a series combination of elements in a series circuit is equal to the resistance of the element or series combination of elements divided by the total resistance of the series circuit and multiplied by the total impressed voltage in figure(1):

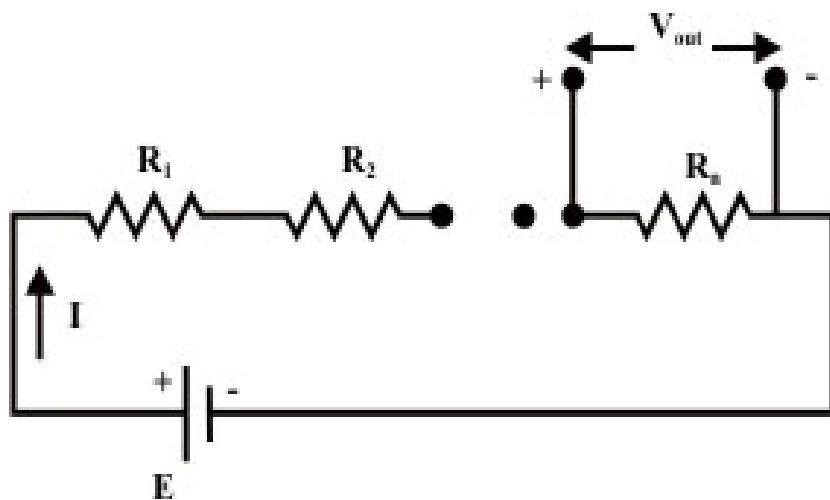


Fig. 1 Voltage Divider

$$V_{out} = IR_n = \frac{E}{R_1 + R_2 + R_3 + \dots + R_n} * R_n \dots\dots\dots(1)$$



Indicates that the voltage across any resistor R_i ($i = 1, 2, \dots, n$) in a series circuit is equal to the applied voltage (E) across the circuit multiplied by a factor— $\frac{R_i}{\sum_{j=1}^n R_j}$

. It should be noted that this expression is only valid if the same current I flows through all the resistors.

Current Divider Rule

The Current Divider Rule (CDR) states that the current through one of two parallel branches is equal to the resistance of the other branch divided by the sum of the resistances of the two parallel branches and multiplied by the total current entering the two parallel branches in figure(2). That is,

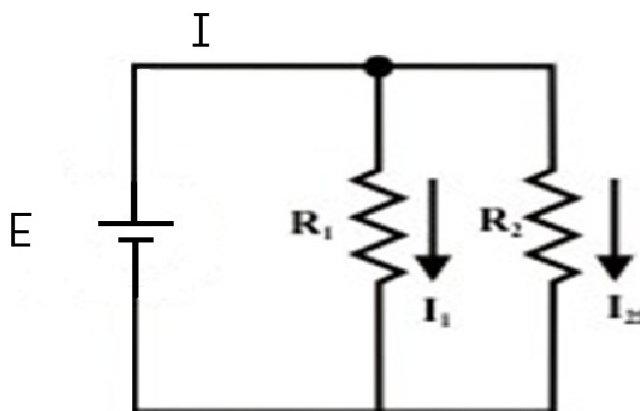


Fig. 2 Current Divider

$$\frac{I_1}{I_S} = \frac{V/R_1}{V(\frac{1}{R_1} + \frac{1}{R_2})} = \frac{R_2}{R_1 + R_2}$$

Or $I_1 = \frac{R_2}{R_1 + R_2} * I_S$



Similarly, the current flowing through the R2 can be obtained as:

$$I_2 = \frac{R_1}{R_1 + R_2} * I_S$$

It can be noted that the expression for I_2 has R_2 on its top line, that for I_1 has R_1 on its top line.

Procedure

Part 1: Voltage Divider Rule

1. Using the DC circuit trainer, connect the circuit shown in Fig. (1), take $E = 10V$, $R_1 = 82\Omega$, $R_2 = 100\Omega$ and $R_3 = 150\Omega$.
2. Measured the voltage and current of " R_1 , R_2 & R_3 ".
3. Exchange the value of resistors as following: $R_1 = 10K\Omega$, $R_2 = 1000\Omega$, $R_3 = 50\Omega$.
4. Repeat step(2), change the value of resistors as following: $R_1 = 30\Omega$, $R_2 = 500\Omega$, $R_3 = 100\Omega$.

Part 2: Current Divider Rule

1. Using the DC circuit trainer, connect the circuit shown in Fig. (2). take $E = 10V$, $R_1 = 82\Omega$ and $R_2 = 100\Omega$.
2. Measured the voltage and current of " R_1 , R_2 ".
3. Exchange the value of resistors as following: $R_1 = 10K\Omega$, $R_2 = 1000\Omega$.
4. Repeat step(2), change the value of resistors as following: $R_1 = 30\Omega$, $R_2 = 500\Omega$.

Discussion

- 1- Comment on your results.
- 2- Compare between the practical and theoretical results.
- 3- When is used VDR and CDR.
- 4- For the circuit shown in Figure(3). Calculate V_{out} , ignoring the internal resistance R_s of the source E . Use voltage division.

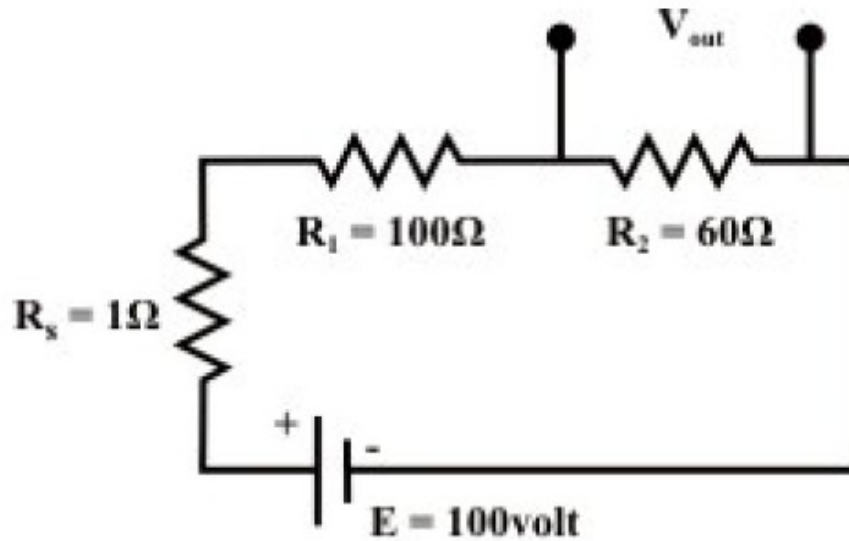


Fig. 3

4 . Determine I_1, I_2, I_3 and I_5 using only current divider formula when $I_4 = 4\text{A}$.

